 


**MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.**

- 1) The carry output of a half-adder circuit can be expressed as \_\_\_\_\_.  
 A)  $C_{out} = AB$                       B)  $C_{out} = A \oplus B$                       C)  $C_{out} = A + B$                       D) None of these
- 2) What is the major difference between half-adders and full-adders?  
 A) Half-adders can only handle single digit numbers.  
 B) Nothing basically; full-adders are made up of two half-adders.  
 C) Full-adders have a carry input capability.  
 D) Full-adders can handle double digit numbers.

- 3) Which of the following is one of the primary functions performed by registers?  
 A) AND                      B) XOR                      C) memory                      D) NOR

- 4) Which of the illustrations below represents the parallel-in serial-out register function?




- A) Figure I.                      B) Figure II.                      C) Figure III.                      D) Figure IV.

- 5) How many flip-flops are required to construct a decade counter?  
 A) 8                      B) 4                      C) 10                      D) 5
- 6) An active-HIGH input S-R latch has a 1 on the S input and a 0 on the R input. What state is the latch in?  
 A)  $Q = 1, \bar{Q} = 0$                       B)  $Q = 0, \bar{Q} = 0$                       C)  $Q = 0, \bar{Q} = 1$                       D)  $Q = 1, \bar{Q} = 1$
- 7) What advantage does a J-K flip-flop have over an R-S flip-flop?  
 A) It has no invalid states.                      B) It has fewer gates.  
 C) It has only one output.                      D) It does not require a clock input.
- 8) What is one disadvantage of an R-S flip-flop?  
 A) It has an invalid state.                      B) It has no Enable input.  
 C) It has no CLOCK input.                      D) It has only a single output.
- 9) Which of the following is correct for a gated D latch?  
 A) Only one of the inputs can be high at a time.  
 B) Q output follows the input D when the ENABLE is high.  
 C) The output complement follows the input when enabled.  
 D) The output toggles if one of the inputs is held high.
- 10) Which symbol is used to identify edge-triggered flip-flops?  
 A) The letter E on the Enable input.                      B) An inverted "L" on the output.  
 C) A bubble on the Clock input.                      D) A triangle on the Clock input.

- 11) Which of the following describes the operation of a positive edge-triggered D flip-flop?
- A) When both inputs are low, an invalid state will exist.
  - B) The output will follow the input on the leading edge of the clock.
  - C) The input is toggled into the flip-flop on the leading edge of the clock and is passed to the output on the trailing edge of the clock.
  - D) If both inputs are high, the output will toggle.

- 12) If both inputs of an S-R flip-flop are low, what will happen when the clock goes high?
- A) The output will toggle.
  - B) An invalid state will exist.
  - C) No change will occur in the output.
  - D) The output will reset.

 
- 13) These waveforms are applied to a gated D latch, which is initially RESET. Which of the areas identified on the Q waveform is incorrect?



- A) Area a
- B) Area b
- C) Area c
- D) Area d

- 14) Flip-flops are normally used for all of the following applications, except \_\_\_\_\_.
- A) data storage
  - B) logic gates
  - C) frequency division
  - D) counting

 - 15) The circuit below can be used as a(n) \_\_\_\_\_.



- A) 8-bit comparator
- B) 4-bit half-adder
- C) dual 4-line multiplexer
- D) 4-bit comparator

- 16) The function  $\overline{A}\overline{B}\overline{C}\overline{D}$  can be decoded with \_\_\_\_\_.
- A) Two 2-input OR gates and two inverters
  - B) Two 2-input OR gates and one inverter
  - C) One 4-input AND gate and two inverters
  - D) One 4-input AND gate and one inverter

- 17) A BCD-to-decimal decoder has \_\_\_\_\_ data input lines and \_\_\_\_\_ data output lines.
- A) 7,9
  - B) 1,10
  - C) 4, 10
  - D) 10,10

- 18) Which of the following is true for IC comparator circuits?
- A) All comparators have outputs for indicating  $A < B$ ,  $A > B$ , and  $A = B$ .
  - B) Comparators can compare only 2 bits at a time.
  - C) Comparators can compare only two values at a time.
  - D) None of these.

- 19) A 1-of-16 decoder IC has \_\_\_\_\_ data input connection(s).
- A) 1
  - B) 16
  - C) 8
  - D) 4

- 20) A multiplexer with four select, or address, lines can select one of \_\_\_\_\_ inputs.  
 A) 15                                      B) 7                                      C) 16                                      D) 3

 


Figure 6-1

- 21) The symbol in Figure 6-1 represents a(n) \_\_\_\_\_.  
 A) Full-adder                                      B) PLD                                      C) AND function                                      D) Half-adder
- 22) Referring to the symbol in Figure 6-1, which set of outputs is very unlikely to ever occur?  
 A)  $\Sigma = 1, C_{out} = 1$                                       B)  $\Sigma = 1, C_{out} = 0$                                       C)  $\Sigma = 0, C_{out} = 1$                                       D)  $\Sigma = 0, C_{out} = 0$

 


Figure 6-2

- 23) Refer to the symbol in Figure 6-2. What are the output when  $A = 1, B = 1, C_{in} = 0$ ?  
 A)  $\Sigma = 1, C_{out} = 0$                                       B)  $\Sigma = 1, C_{out} = 1$                                       C)  $\Sigma = 0, C_{out} = 1$                                       D)  $\Sigma = 0, C_{out} = 0$
- 24) The symbol in Figure 6-2 represents a(n) \_\_\_\_\_.  
 A) Full-adder                                      B) And function                                      C) Half-adder                                      D) PLD

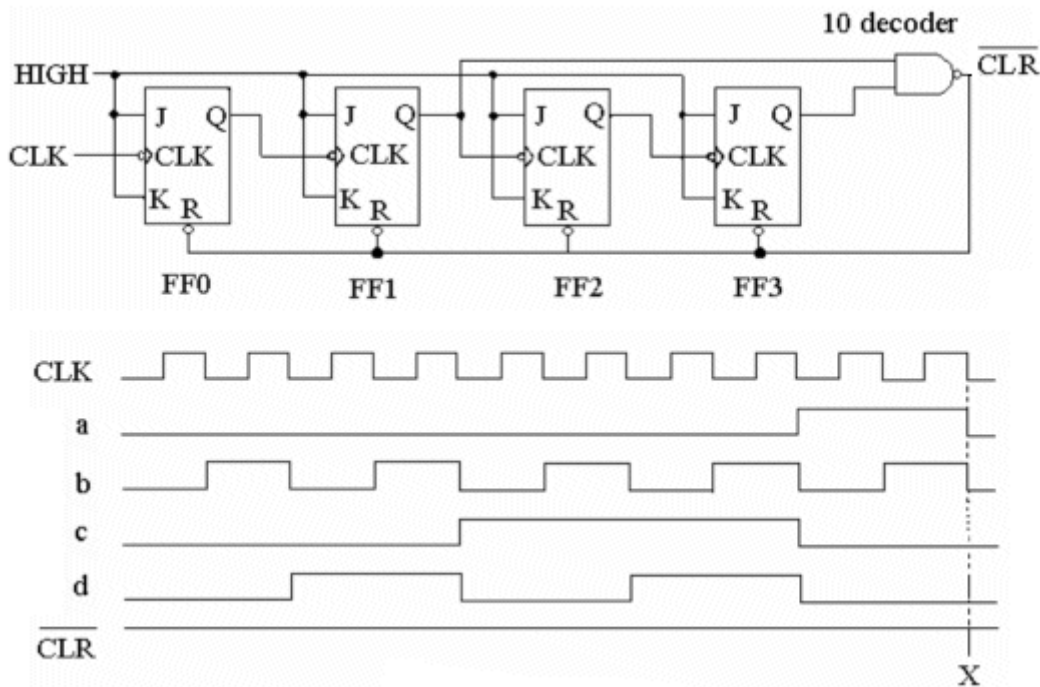


Figure 8-2

- 25) Which of the waveforms shown in Figure 8- represents the output of FF2?  
 A) waveform a                                      B) waveform b                                      C) waveform c                                      D) waveform d
- 26) The circuit in Figure 8-2 is a(n) \_\_\_\_\_.  
 A) three-bit synchronous binary counter                                      B) four-bit asynchronous binary counter  
 C) two-bit asynchronous binary counter                                      D) eight-bit asynchronous binary flip-flop

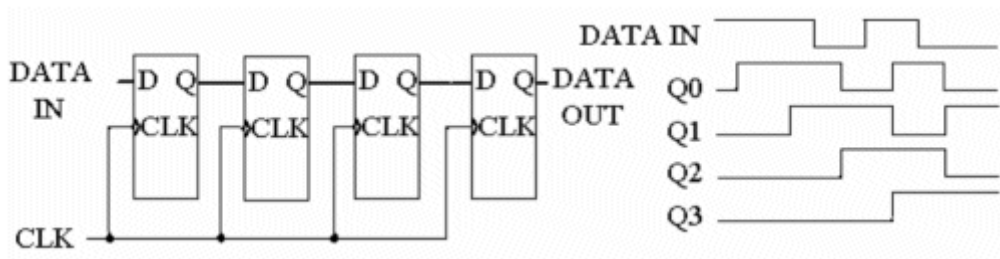


Figure 9-1

- 27) After the data input shown in Figure 9-1 has been entered into the register, what values are stored in Q3, Q2, Q1, and Q0 respectively?  
 A) 1 0 0 1                      B) 0 1 0 1                      C) 1 1 0 1                      D) 1 0 1 0
- 28) How many clock cycles are required to enter the data into the register in Figure 9-1?  
 A) 32                                B) 4                                C) 5                                D) 31
- 29) How many data bits can be stored in the register shown in Figure 9-1?  
 A) 4                                B) 32                                C) 5                                D) 31

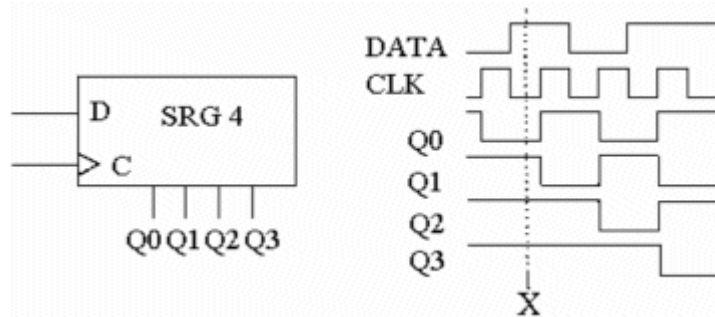


Figure 9-2

- 30) Refer to the circuit and waveforms in Figure 9-2. What is the value of the data stored in Q3, Q2, Q1 and Q0 respectively at time 'X'?  
 A) 1 1 1 0                      B) 0 1 0 1                      C) 0 1 1 0                      D) 0 1 1 1
- 31) Refer to the circuit and waveforms in Figure 9-2. What is the value of the data stored in Q3, Q2, Q1 and Q0 respectively after four clock cycles?  
 A) 0 1 1 0                      B) 1 0 1 0                      C) 0 0 0 0                      D) 0 1 0 1


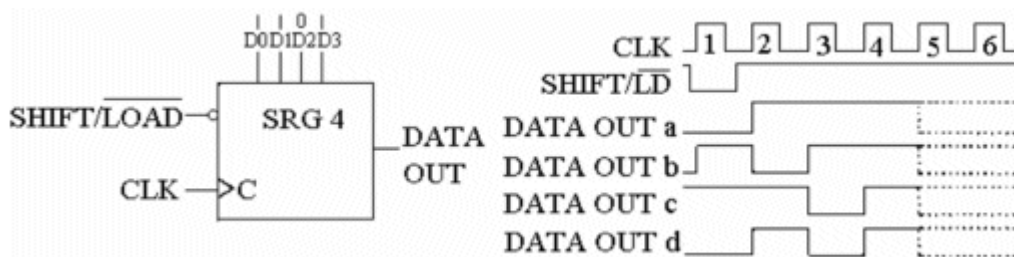


Figure 9-3

- 32) Which of the DATA OUT waveforms in Figure 9-3 is correct?  
 A) DATA OUT a.                      B) DATA OUT b.                      C) DATA OUT d.                      D) DATA OUT c.
- 33) The circuit shown in Figure 9-3 is a \_\_\_\_\_.  
 A) serial-in parallel-load register                      B) demultiplexer  
 C) multiplexer    D) parallel-in serial-out register

TRUE/FALSE. Write 'T' if the statement is true and 'F' if the statement is false.

 - 34) Shift registers are used to store and transfer data.
- 35) A serial-in serial-out shift register transfers data from one line of a parallel bus to another line one bit at a time.
- 36) A J-K flip-flop can be used as a divide-by-two frequency divider with an output duty cycle of 50%.
- 37) Parallel-in parallel-out registers have parallel input and output busses.
- 38) Bidirectional shift registers can shift data either right or left.
- 39) The term *synchronous* refers to events that do not occur at the same time.
- 40) Basic counters can be cascaded in parallel to increase the number of data bits that the counter can handle.
- 41) The symbol for an edge-triggered flip-flop has a triangle on its clock input.
- 42) A D flip-flop is constructed by connecting an inverter between the Set and Clock terminals.
- 43) The J-K flip-flop eliminates the invalid state by toggling when both inputs are high during the transition of the clock signal.
- 44) In binary addition,  $1 + 1 = 10$
- 45) The waveforms for this J-K flip-flop indicate the circuit is operating properly.



- 46) A group of four bits is called a byte.
- 47) Full-adders do not provide for a carry input or a carry output.
- 48) A multiplexer has multiple inputs and a single output.
- 49) A demultiplexer has multiple inputs and a single output.
- 50) A half-adder has no carry-in bit.